Ex. No. 5

Design of Single phase Half wave and Full wave Rectifiers

Aim: To verify and obtain the output wave form of single phase half-wave and full-wave nectifier circuit in capture CIS software.

Apparatus/Tool required:


ORCAD / PSpice simulator -> Diode Library - D1N4002/4007, Source Library - Vsin & Ground (GND) - 0(zero) Analog Library - R

Simulation Settings: Analysis Type - Time Domain


Run to time: 40ms (for 2 cycles)

Circuit Diagram:


Single phase Half - wave Rectifier

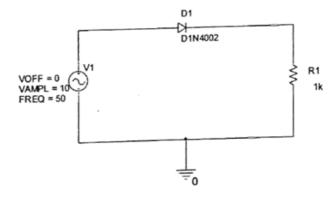


Single phase Full - Wave Rectifier

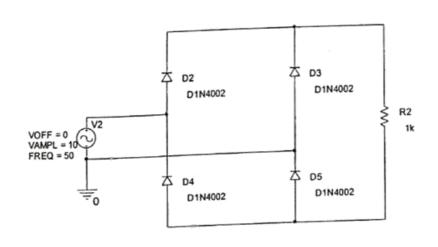



Single phase Half-wave Rectifier:

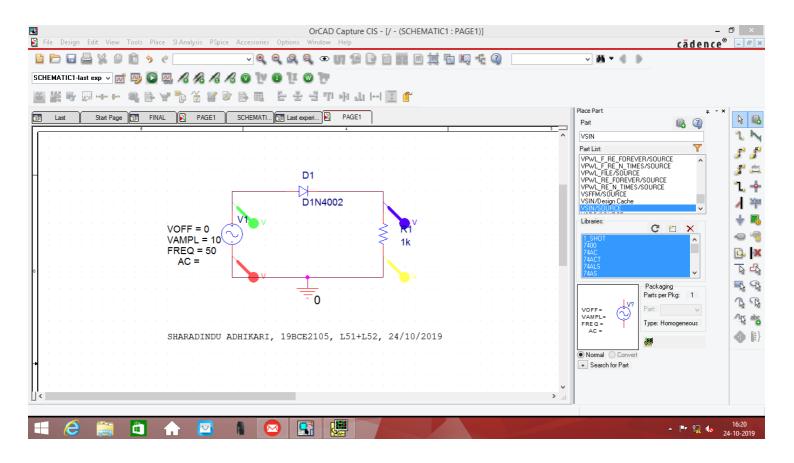

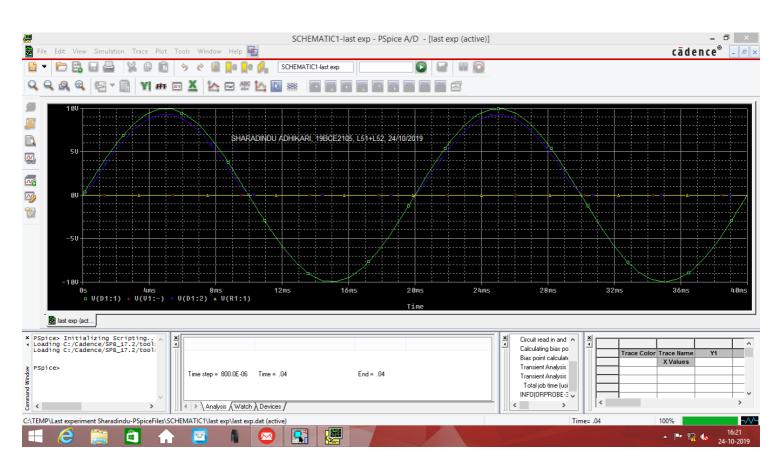


Single phase Full-wave Rectifier:

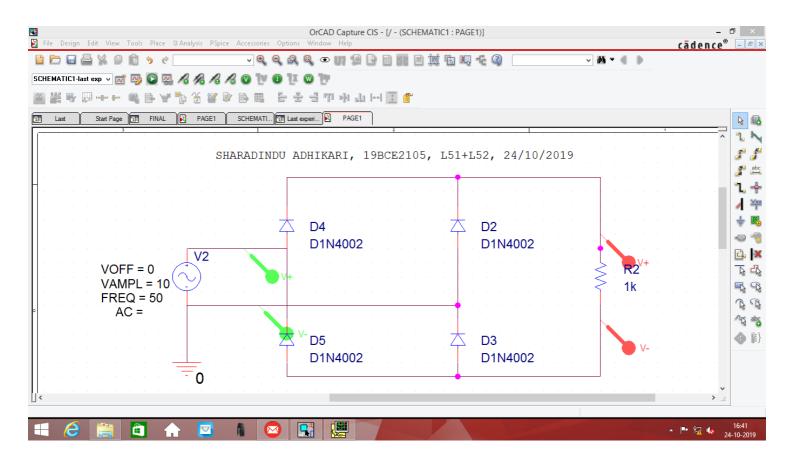

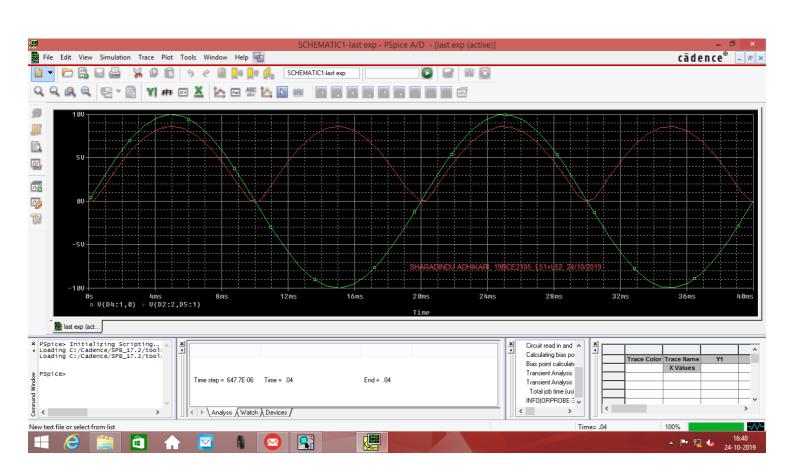

Procedure:

Model Graph:

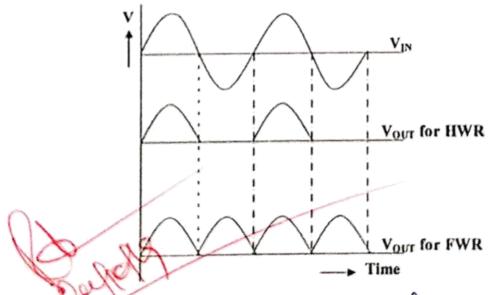

rectifier circuit output waveform have been obtained and verified in simulation [Capture CIS] experiment:

Inference

Reg. No: 19 BCE 2105 Name: SHARADIN DU 4. Date: 24/10/2019