

Verification of NETWORK THEOREMS

(Maximum Power Transfer Theorem)


Aim: To verify the Maximum power Transfer Theorem for the given network by theoretical values and simulation values.

Apparatus/Tool required:

ORCAD / Capture CIS --> Analog Library - R,
Source Library - Vdc, Idc &
Ground (GND) - 0 (zero)

Simulation Settings: Analysis Type - Bias Point





Circuit Diagram

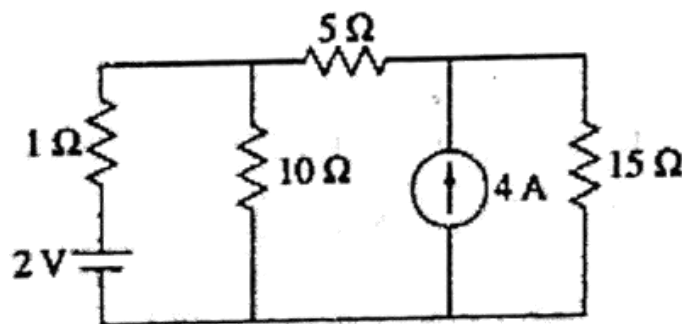

Statement: Maximum Power Transfer Theorem


In a linear bilateral network, the maximum power is transferred from the source to the load when the source resistance must be equal to load resistance.

■ Circuit diagram :-

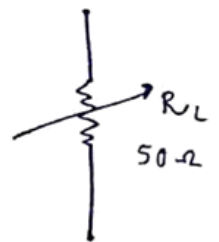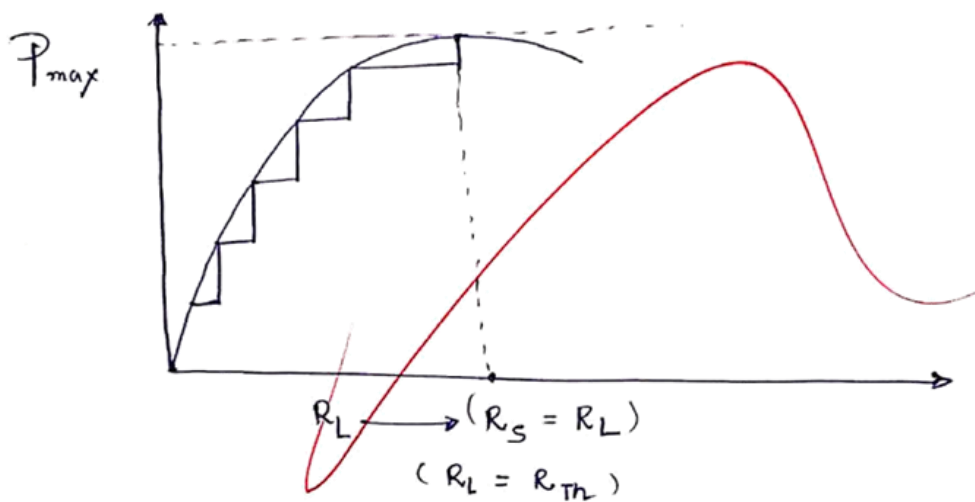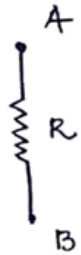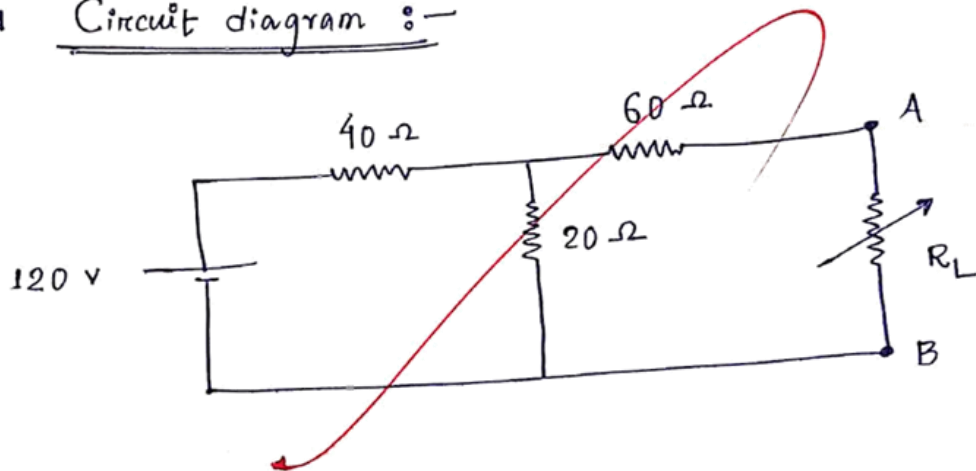

Manual Calculations:

To Find V_{th} :

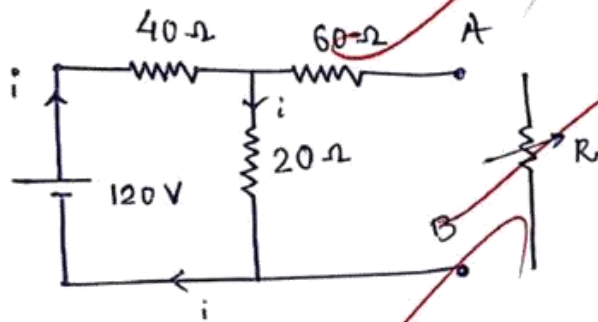

$$i = \frac{V}{R_T}$$

$$i = \frac{120}{(40 + 20)} \text{ A}$$

$$= \frac{120}{60} \text{ A}$$


$$= 2 \text{ A}$$

$$\therefore V_{20\Omega} = i_{20\Omega} \times R_{20\Omega}$$

$$= (2 \times 20) \text{ V}$$

$$\therefore V_{oc} = V_{Th} = 40 \text{ Volts.}$$

To Find R_{th} :

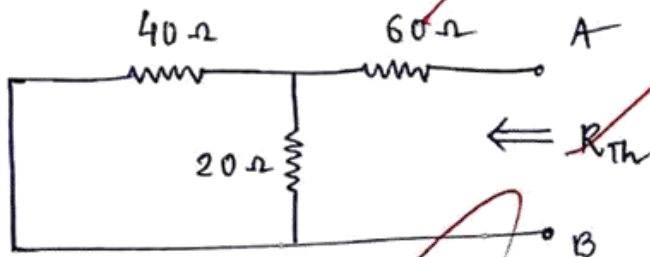

$$R_{AB} = R_i = R_{Th}$$

$$(40 \parallel 20) + 60 \Omega$$


$$= \frac{40 \times 20}{40 + 20} + 60 \Omega$$

$$= 13.33 + 60 \Omega$$

$$\therefore R_{Th} = 73.33 \Omega$$

$$\therefore R_{Th} = R_L = 73.33 \Omega$$

To Find Power:

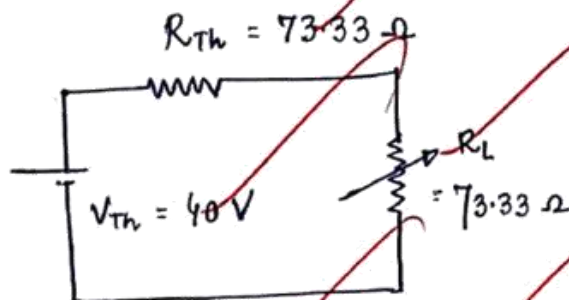

$$i_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{40}{73.33 + 73.33} \text{ A}$$


$$\therefore i_L = 0.27 \text{ Amps}$$

$$\therefore P_L = i_L^2 \cdot R_L = (0.27)^2 \times 73.33 \text{ Watts}$$


$$\therefore P_L = 5.45 \text{ Watts}$$

Simulation Circuit:


To Find V_{th} :

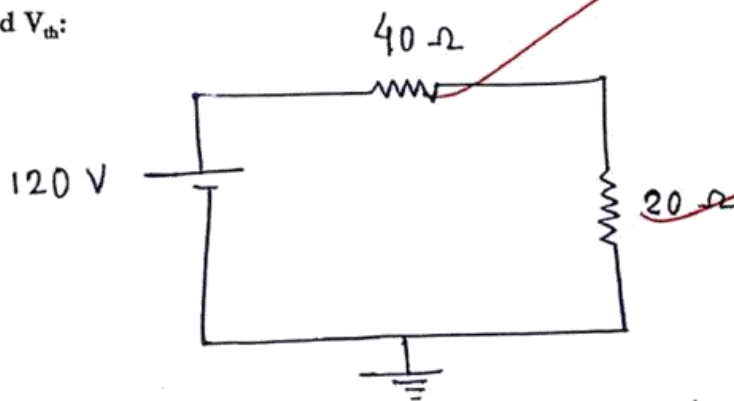

To Find R_{th} :

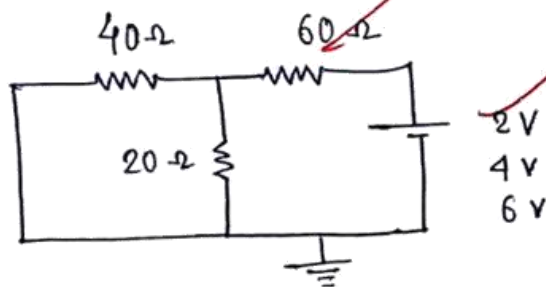

To Find Power:

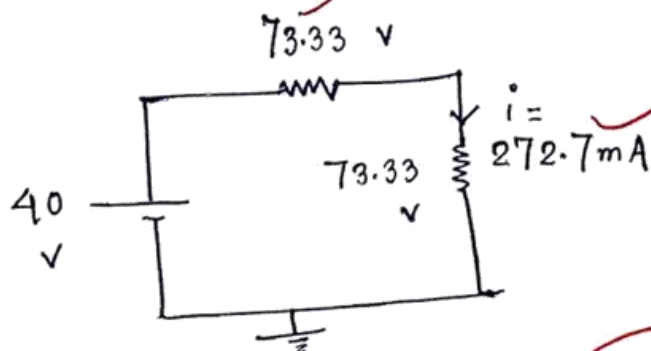


V (volt)	i (mA)	R (Ω)
2	27.27	73.34
4	54.55	73.327
6	81.82	73.33

$$P_{avg} = \frac{73.34 + 73.327 + 73.33}{3} \text{ W}$$



$$= 73.3323 \text{ W}$$


Simulation Circuits:

- To find V_{th} :

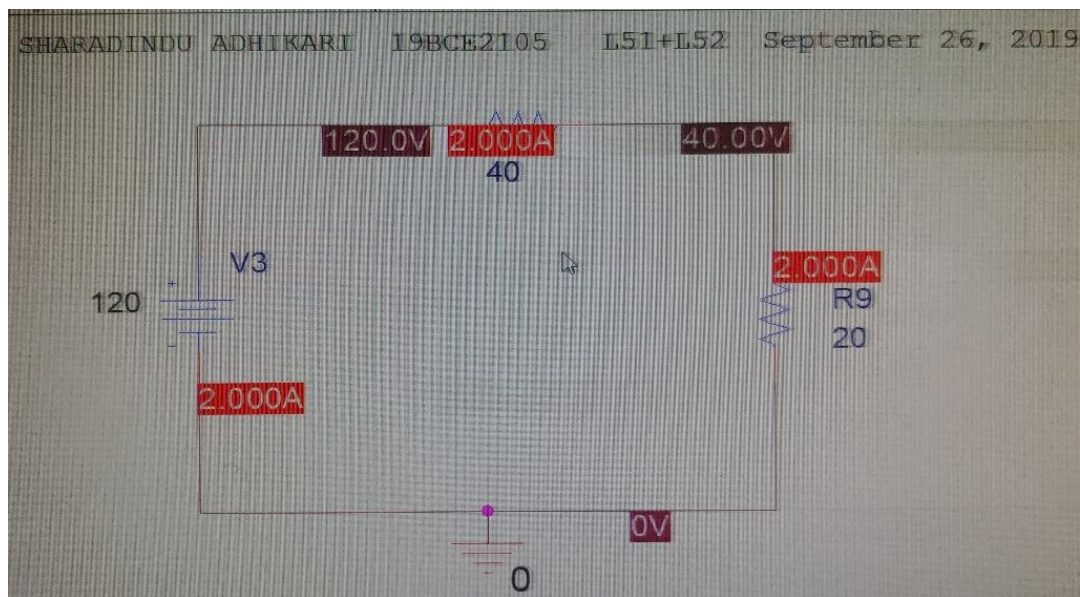


- To find R_{th} :

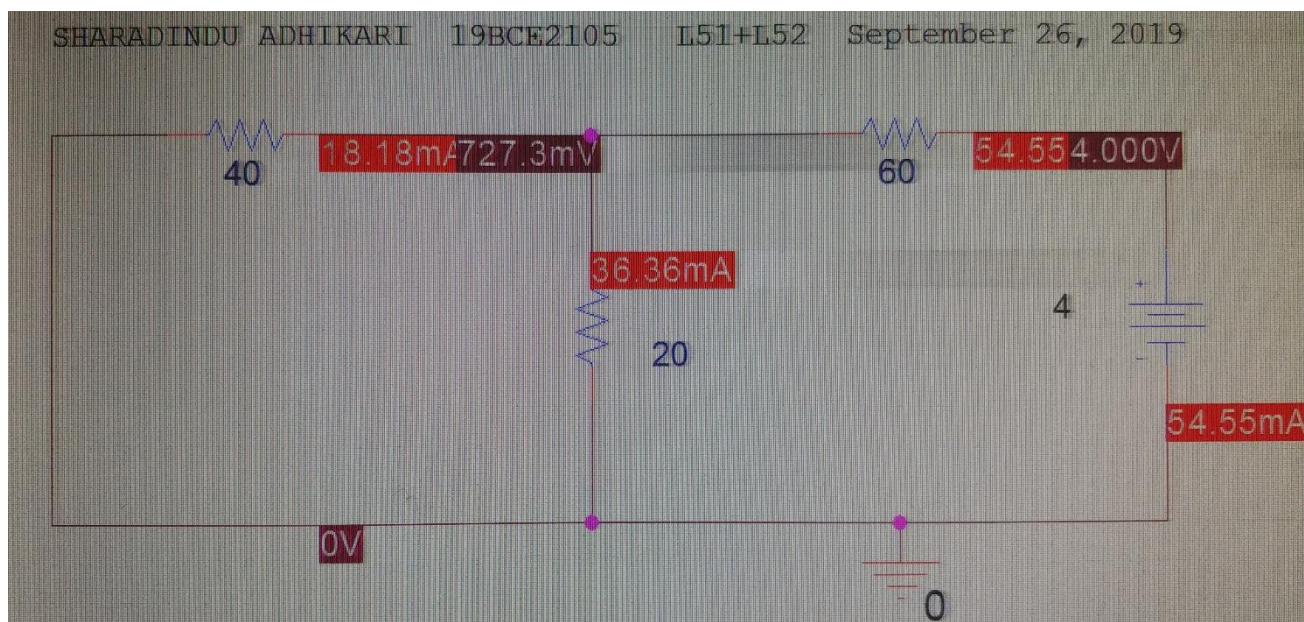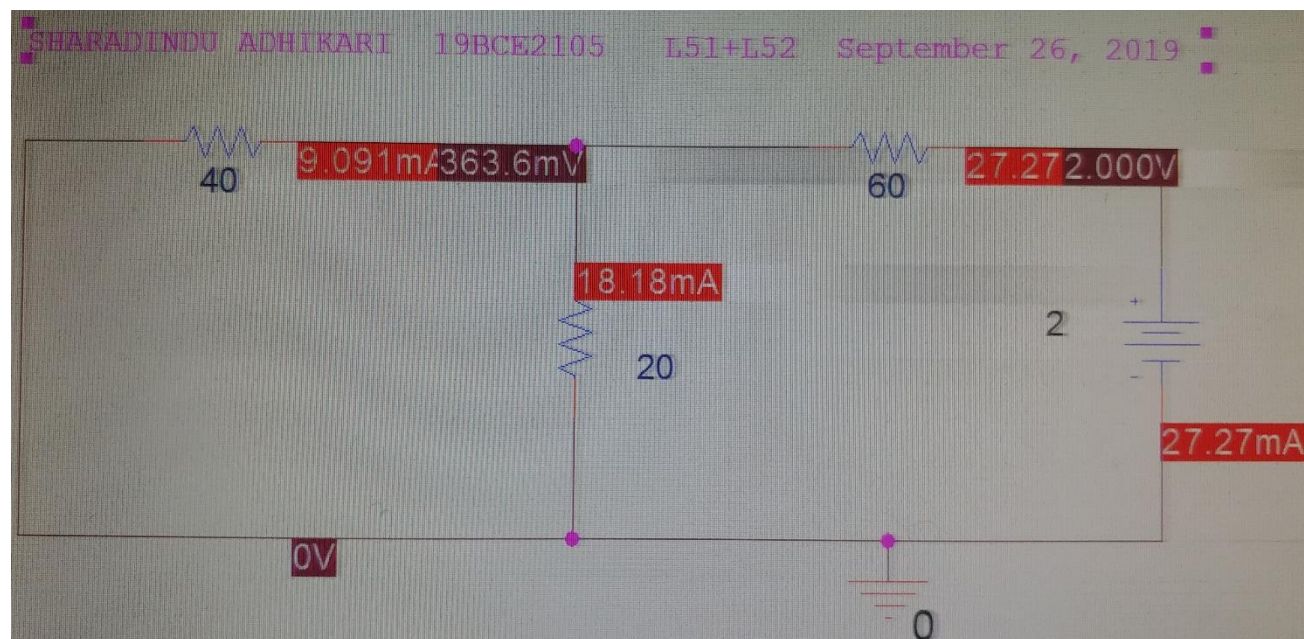

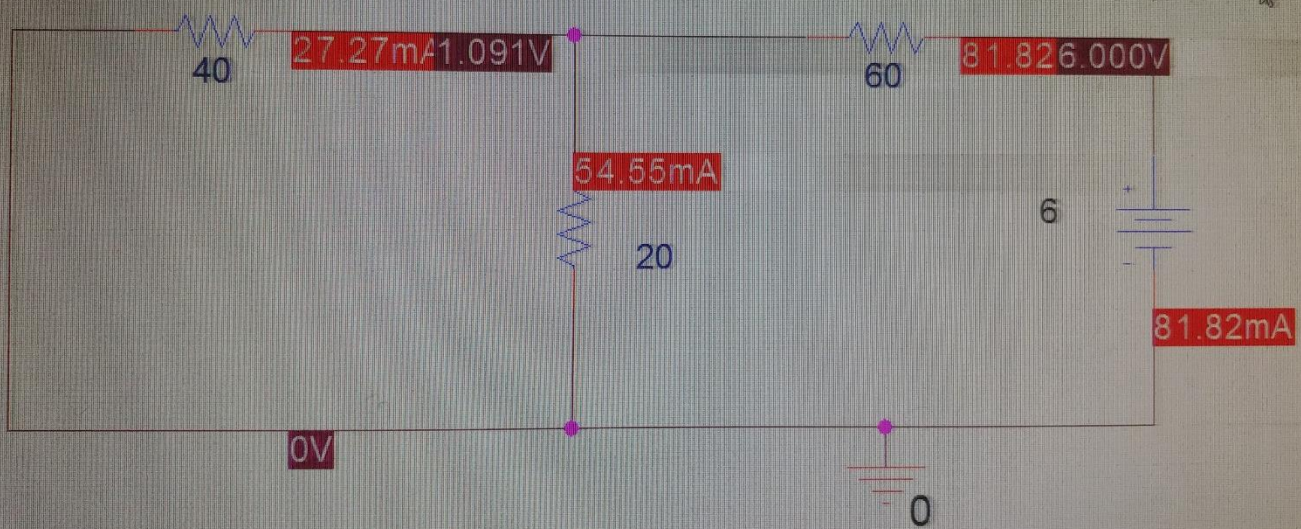

- To find Power:

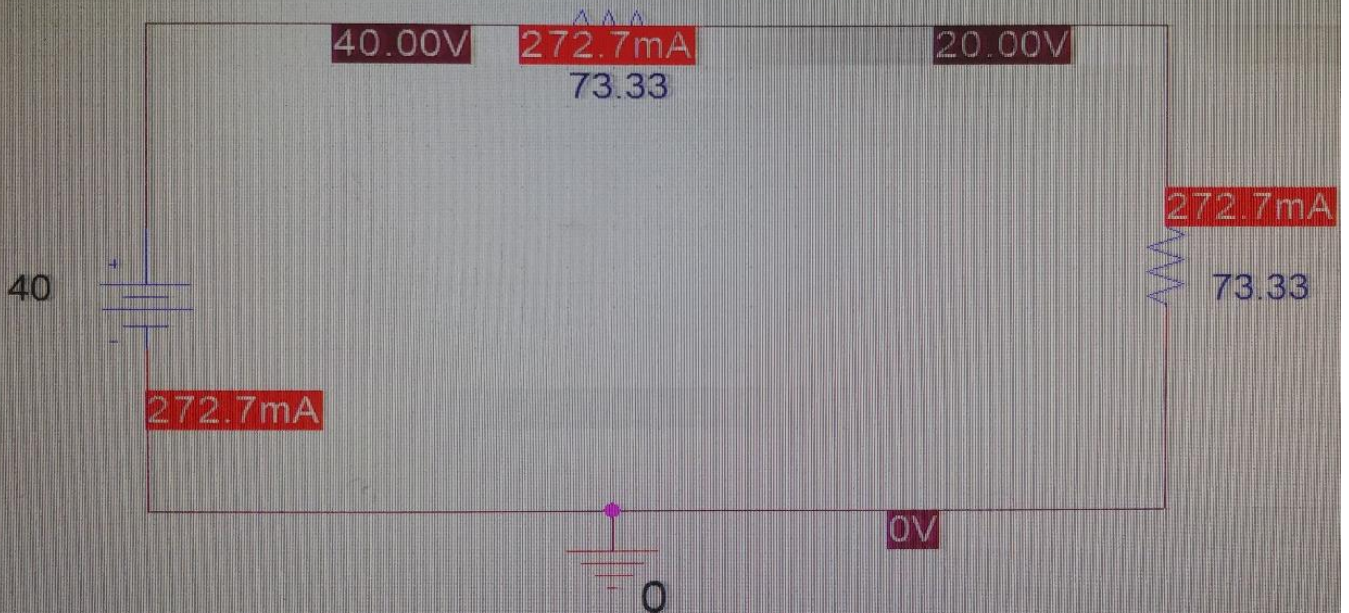

Procedure:

26/9/19
Deepti

Result: The maximum power transfer Theorem have been verified for the given network by theoretical & simulation values, and the following results are tabulated:

Maximum Power Transfer Theorem

parameters

Manual Calculations

Simulated Result

parameters	Manual Calculations	Simulated Result
V_{th}	40 V	40 V
R_{th}	73.33 Ω	73.3323 Ω
i_L	0.27 A	0.2727 A
P_{max}	5.45 W	5.455 W

Reg. No: 19 BCE 2105 Name: SHARADINDU A Date: 26/9/2019