

## Design of Half Adder and Full Adder circuits

**Aim:** To verify the truth tables of Half Adder and Full Adder circuit and its corresponding <sup>output</sup> waveforms in Capture CIS.

### Apparatus/Tool required:

ORCAD / PSpice simulator - > 7400 Library - 7408, 7432 & 7486  
Source Library - Digclock


Simulation Settings: Analysis Type - Time Domain

Run to time: 4ms (for Half Adder)


Run to time: 8ms (for Full Adder)

### Circuit Diagram:

#### Half - Adder Circuit


 


#### Full - Adder Circuit

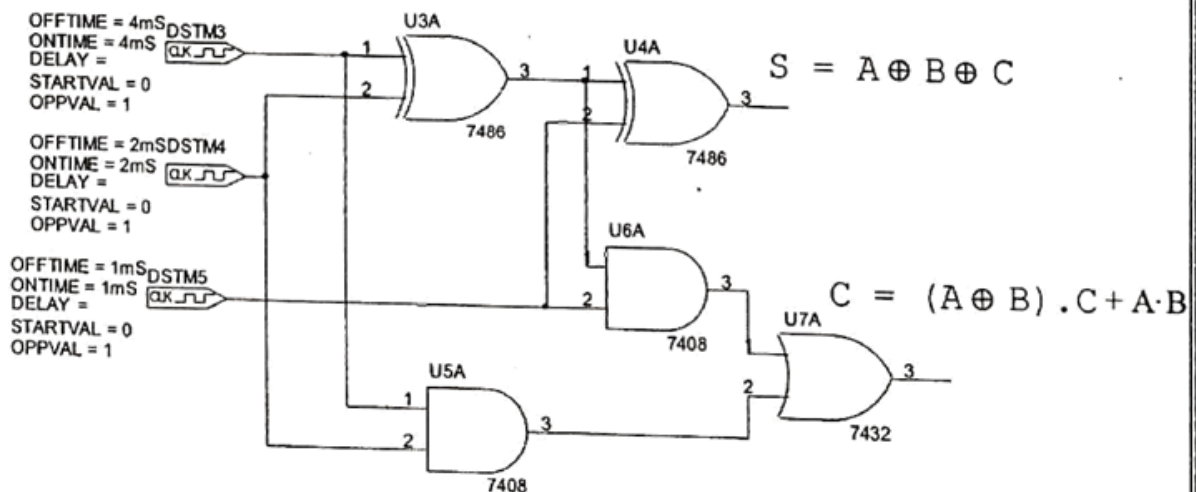





## Half-Adder Circuit:

 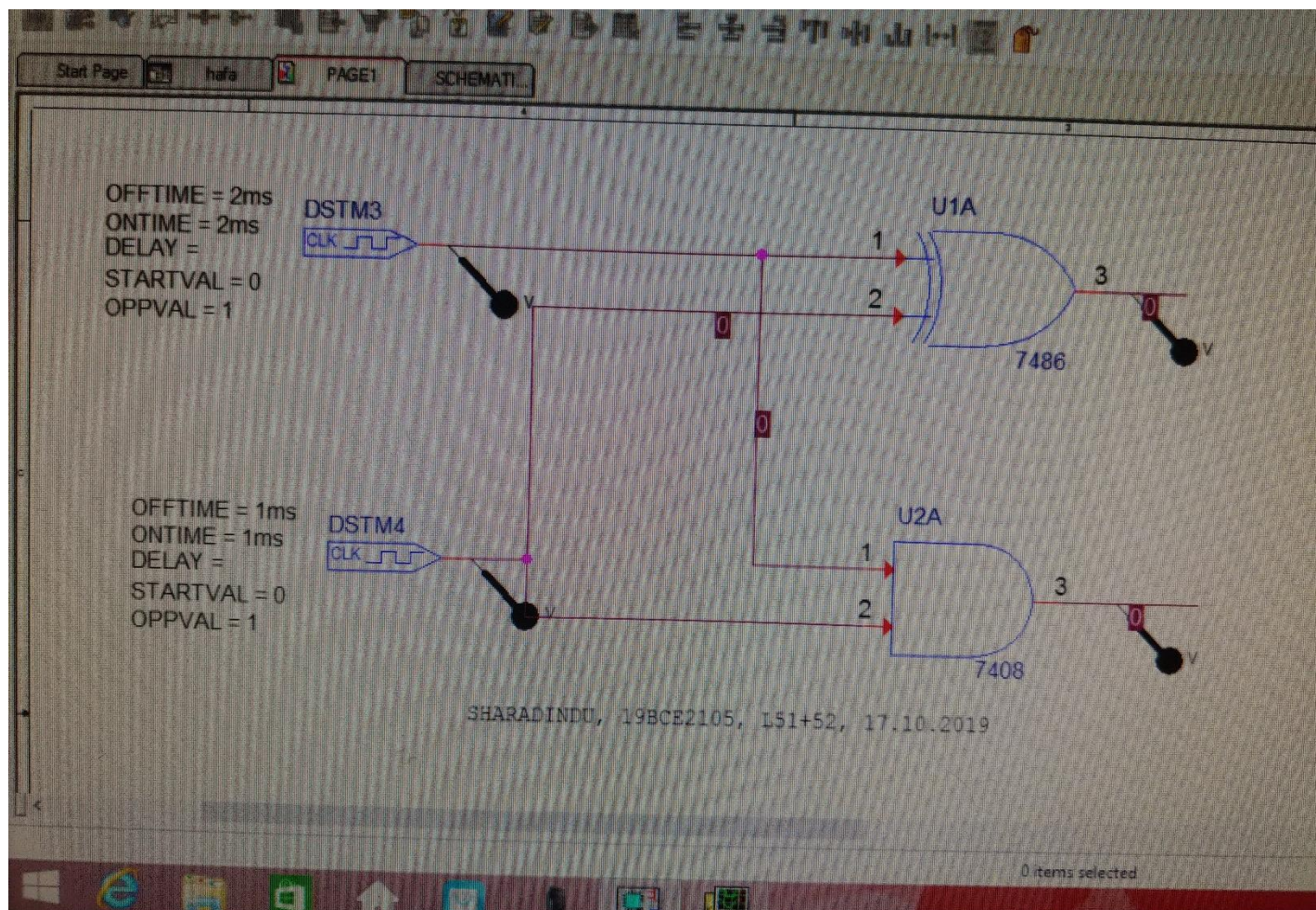



## Full-Adder Circuit:

 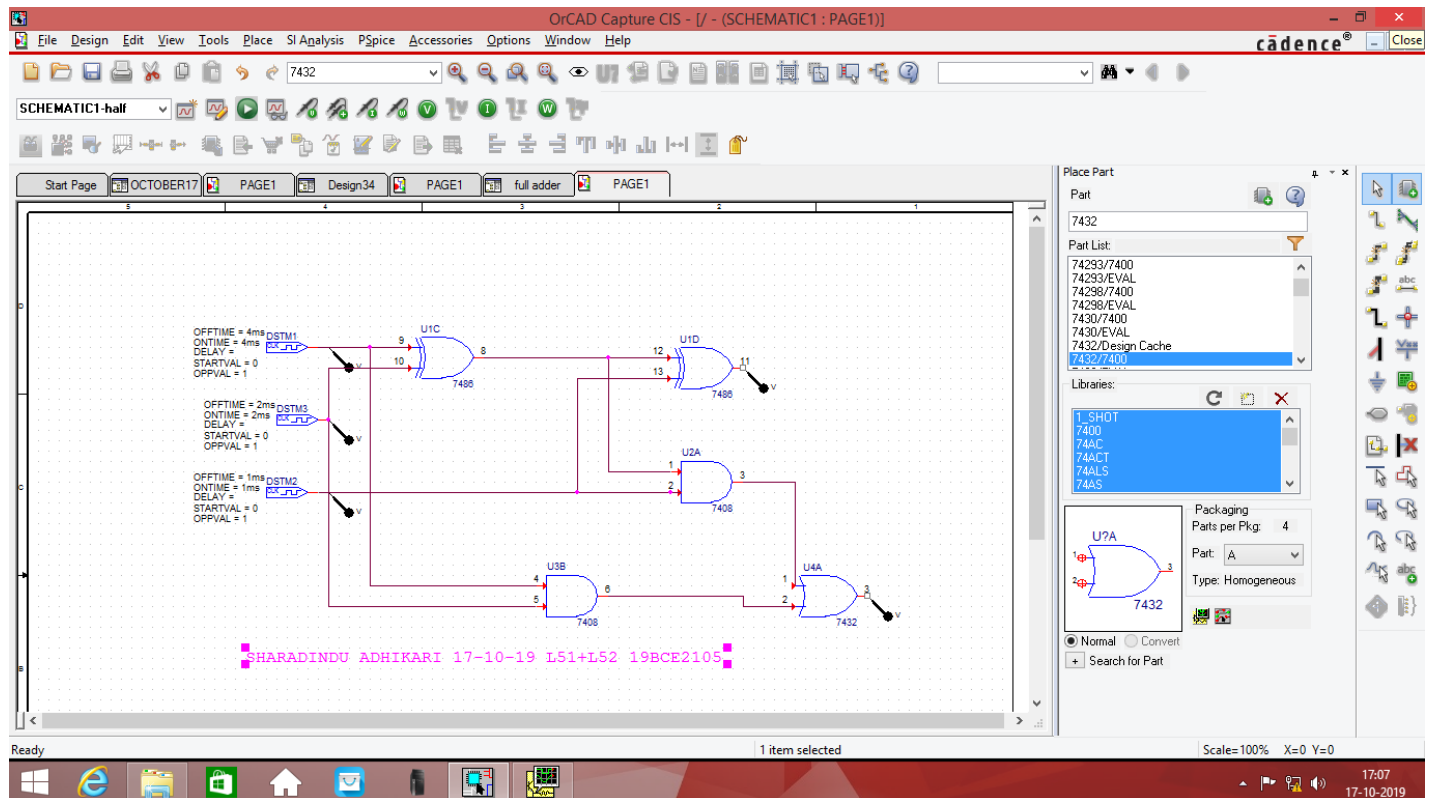

## Theory:


### Half Adder Circuit:

Truth Table

A	B	$S=A \oplus B$	$C=A.B$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### Model Timing Diagram:

#### Half-Adder

 


## Full Adder Circuit

Truth Table

A	B	C	$S = A \oplus B \oplus C$	$C = (A \oplus B).C + A.B$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Model Timing Diagram:

### Full - Adder

 

**Procedure:**

**Result:**

~~The half adder and full adder circuit truth tables and output wave forms have been verified in simulation waveforms~~

→ The half adder and full adder experiments have been performed using Capture CIS.

~~Inference~~

The truth table and its corresponding waveforms have been verified!

17/10/19  
Sharadindu A.

Reg. No: 19 BCE 2105 Name: SHARADINDU A. Date: 17/10/19