

EEE 1001

Digital Assignment - 1


SHARADINDU ADHIKARI

19 BCE 2105

slot- A1 ; SJT 322

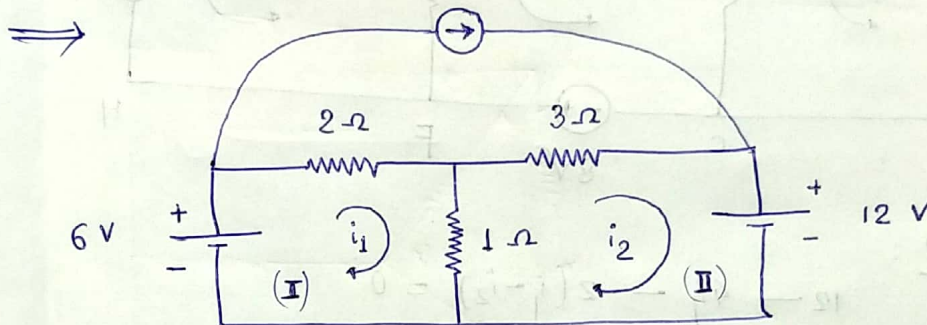Q1.

For the circuit shown in figure, find the current in different branches of resistors.



We have,

$$6 - 2(i_1 - 2) - 1(i_1 - i_2) = 0$$

$$-1(i_2 - i_1) - 3(i_2 - 2) - 12 = 0$$

$$\therefore 6 - 2i_1 + 4 - i_1 + i_2 = 0 \quad \text{--- (I)}$$

$$\Rightarrow 6 - 3i_1 + 4 + i_2 = 0$$

$$\Rightarrow -4i_2 + i_1 = 6 \quad \text{--- (II)}$$

$$i_2 - 3i_1 = -10 \quad \text{--- (I)}$$

Solving eqⁿs (I) and (II), we get:

$$i_1 = 3.090 \text{ A}$$

$$i_2 = -0.727 \text{ A}$$

$$\therefore i_{2\Omega} = -(i_1 - 2)$$

$$= -(3.090 - 2) \text{ A}$$

$$\text{and } i_{1\Omega}$$

$$\Rightarrow i_{2\Omega} = -1.09 \text{ A}$$

$$= -1(i_1 - i_2)$$

$$= -1(3.090 + 0.727) \text{ A}$$

$$\text{--- (II)}$$


$$i_{3\Omega} = -3(i_2 - 2)$$

$$= -3(-0.727 - 2) \text{ A}$$

$$i_{1\Omega} = -3.817 \text{ A}$$

$$\Rightarrow i_{3\Omega} = 2.181 \text{ A}$$

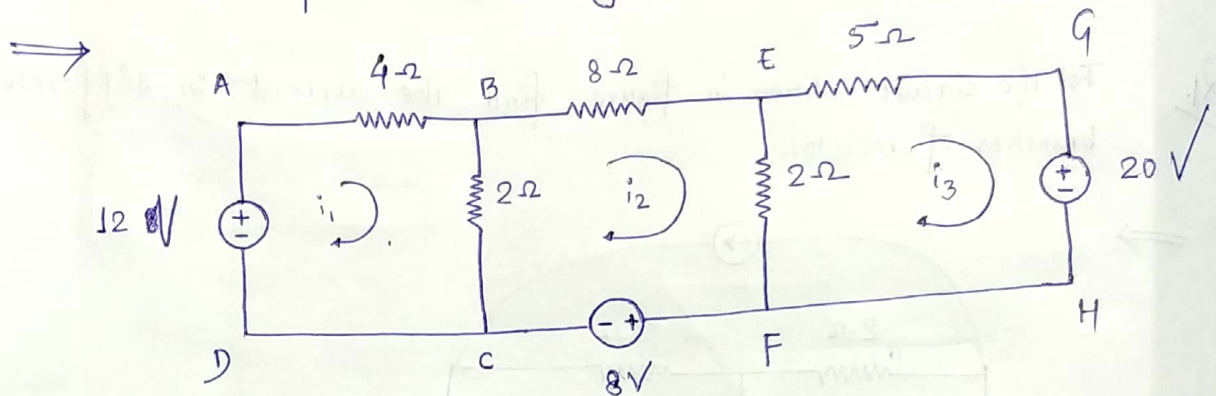Q.2. For the circuit shown in figure, find the mesh currents and the power observed by the 8Ω resistor.



Loop ABCD:

$$12 - 4i_1 - 2(i_1 - i_2) = 0$$

$$\Rightarrow 12 - 6i_1 + 2i_2 = 0$$

$$\Rightarrow 3i_1 - i_2 = 6 \quad \text{--- [1]}$$

Loop BEFC:

$$-2(i_2 - i_1) - 8i_2 - (i_2 - i_3) \cdot 2 - 8 = 0$$

$$\Rightarrow -12i_2 + 2i_1 + 2i_3 = 8$$

$$\Rightarrow i_1 - 6i_2 + i_3 = 4 \quad \text{--- [2]}$$

Loop EGFH:

$$-(i_3 - i_2) \cdot 2 - 5i_3 - 20 = 0$$

$$\Rightarrow 2i_2 - 7i_3 = 20 \quad \text{--- [3]}$$

Solving eq^s [1], [2], & [3], we get:

$$i_1 = 1.699 \text{ A} ; \quad i_2 = -0.902 \text{ A}$$

$$i_3 = -3.115 \text{ A}$$

\therefore power across 8Ω resistor,

$$P_{8\Omega} = i_2^2 R$$


$$= (-0.902)^2 \times 8 \text{ W}$$

$$P = 6.508 \text{ W}$$

ans.

$$\Rightarrow 3v_1 - 3v_2 = 5v_2 - 3v_3 + 199.8$$
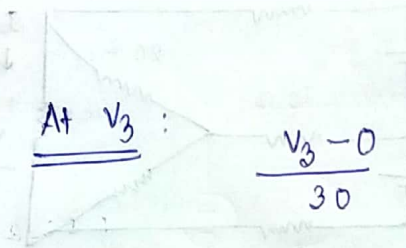
$$\Rightarrow 3v_1 - 8v_2 + 3v_3 = 199.8 \quad \text{--- (2)}$$



At v_3 :

$$\frac{v_3 - 0}{30} = \frac{v_1 - v_3}{20} + \frac{v_2 - v_3}{20}$$

$$\Rightarrow 2v_3 = 3(v_1 + v_2 - 2v_3)$$

$$\Rightarrow 3v_1 + 3v_2 - 8v_3 = 0 \quad \text{--- (3)}$$

Solving eqⁿs (1), (2), and (3), we get

$$v_1 = 18.16 \quad \checkmark$$

$$v_2 = -18.16 \quad \checkmark$$

$$v_3 = 0 \quad \checkmark$$

Also $I = 1.816 \text{ A}$


$$V_{cd} = v_1 - v_2 = 18.16 - (-18.16) \quad \checkmark$$

$$\therefore V_{cd} = 36.32 \text{ V}$$

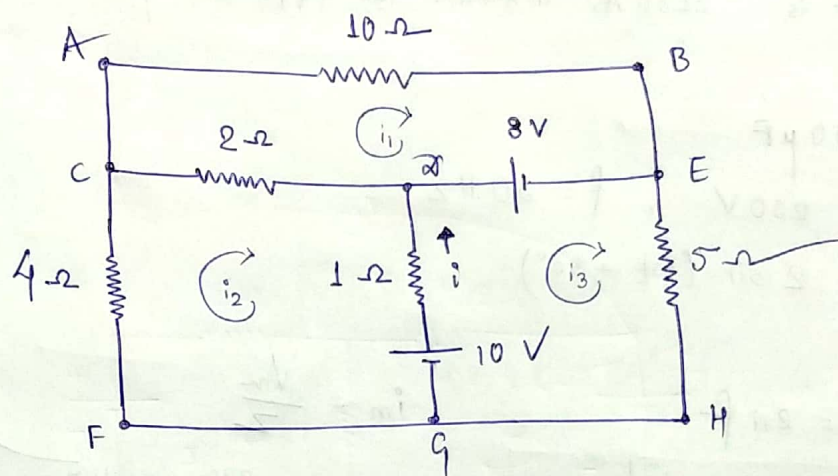Q4.

19BCE2105

Apply mesh analysis to find i in the circuit shown in the figure.



In Loop ABEC,

$$-10i_1 + 8 - 2(i_1 - i_2) = 0$$

$$\Rightarrow 6i_1 - i_2 = 4 \quad \text{--- (1)}$$

In Loop FCDE,

$$-4i_2 - (i_2 - i_1)2 - (i_2 - i_3) - 10 = 0$$

$$\Rightarrow 2i_1 - 7i_2 + i_3 = 10 \quad \text{--- (2)}$$

In Loop GDEM,

$$10 - (i_3 - i_2) - 8 - 5i_3 = 0$$

$$\Rightarrow i_2 - 6i_3 = -2 \quad \text{--- (3)}$$

Solving (1), (2), & (3), we've:

$$i_1 = 0.453 \text{ A}$$

$$i_2 = -1.282 \text{ A}$$

$$i_3 = 0.119$$

$$\therefore i = i_3 - i_2$$

$$\boxed{i = 1.401 \text{ A}} \quad \text{ans}$$

Q5. A coil of resistance $R \Omega$ and inductance L henrys, is connected in series with a $50 \mu F$ capacitor. If the supply voltage is $230 V$ at $50 Hz$ and the current flowing in the circuit is $2 \angle 30^\circ A$, determine the different parameters: —

$$C = 50 \mu F$$

$$V_m = 230 V, \quad f = 50 Hz$$


$$i = 2 \sin(\omega t + 30^\circ)$$

$$\textcircled{1} \quad \omega = 2\pi f$$

$$\Rightarrow \omega = 314 \text{ rad/s}$$

$$i_m = \frac{V_m}{Z}$$

$$\Rightarrow Z = \frac{230}{2} = 115$$

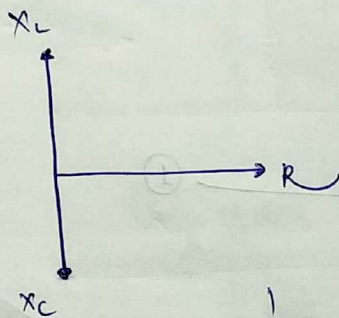

$$\phi = 30^\circ$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\Rightarrow X_L - X_C = \frac{R}{\sqrt{3}}$$

$$X_C = \frac{1}{\omega C} = 63.7$$

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$\Rightarrow Z^2 = R^2 + \left(\frac{R}{\sqrt{3}}\right)^2$$

$$\Rightarrow (115)^2 = R^2 + \frac{R^2}{3}$$

$$\Rightarrow R^2 = (115)^2 \times \frac{3}{4}$$

$$\Rightarrow \boxed{R = 99.6 \Omega}$$

$$X_L = X_C + \frac{R}{\sqrt{3}} = 121.20$$

$$\Rightarrow \omega L = 121.20$$

$$\Rightarrow L = \frac{121.20}{314}$$

$$\therefore \boxed{L = 0.386 H}$$

$$(ii) \quad V_L = i X_L$$

$$= 2 \times 121.2 \times \sin(314t + 30^\circ)$$



$$= 242.2 \sin(314t + 30^\circ)$$

$$(iii) \quad V_C = i X_C$$



$$= 63.7 \times 2 \times \sin(314t + 30^\circ)$$

$$= 127.4 \sin(314t + 30^\circ)$$

$$(iv) \quad \phi = 30^\circ$$

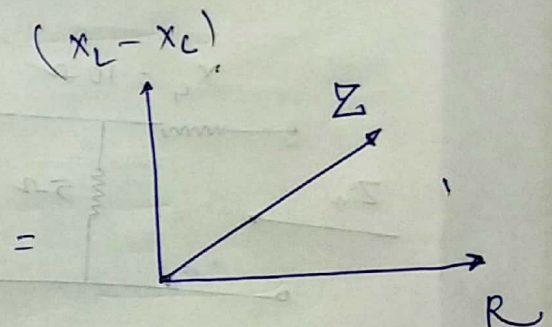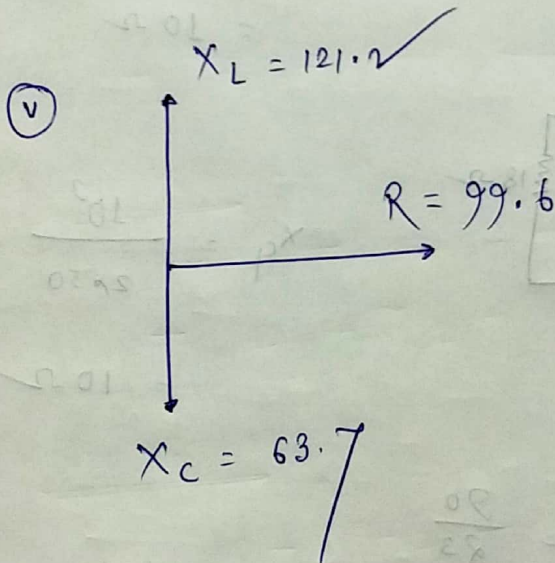

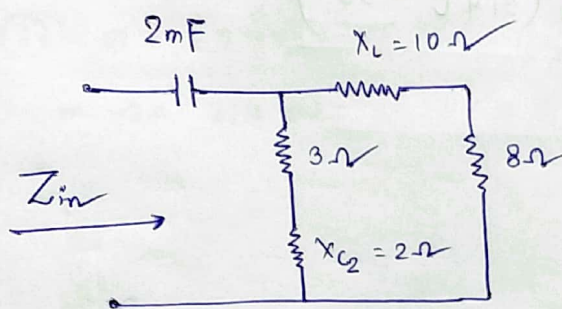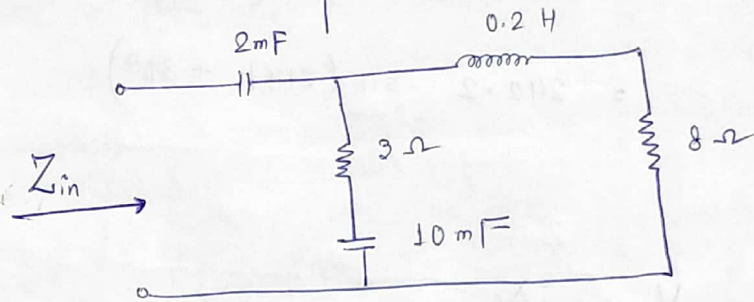Q6. Find the input impedance of the circuit shown in figure. Assume that the circuit operates at $\omega = 50 \text{ rad/s}$.




$$X_{C2} = \frac{10^3}{10 \times 50} \Omega$$

$$= 2 \Omega$$


$$X_L = 0.2 \times 50 \Omega$$

$$= 10 \Omega$$

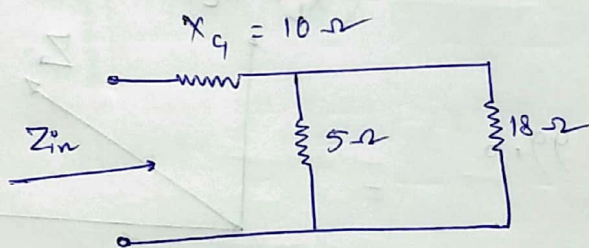

$$X_C = \frac{10^3}{2 \times 50} \Omega$$

$$= 10 \Omega$$

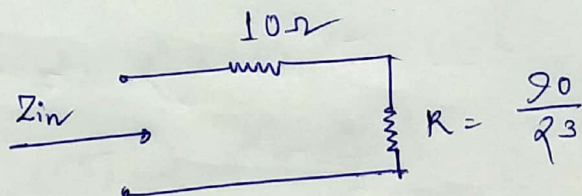






$$R = \frac{18 \times 5}{18 + 5} \Omega$$

$$= \frac{90}{23} \Omega$$

$$\therefore Z_{in} = 10 + \frac{90}{23} \Omega$$

$$= 13.91 \Omega \quad (\text{ans})$$

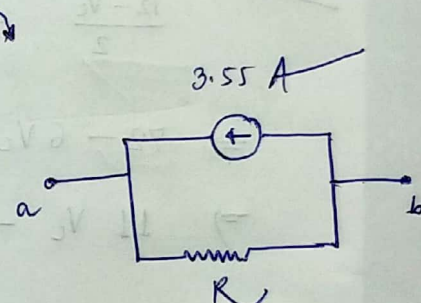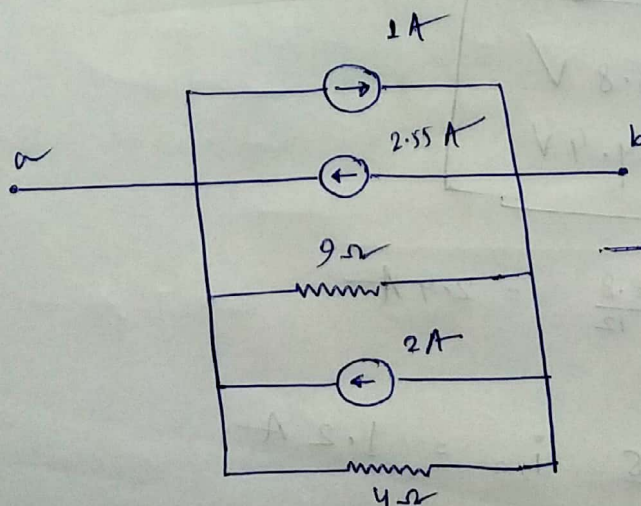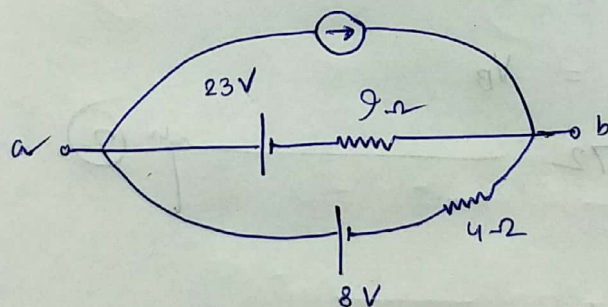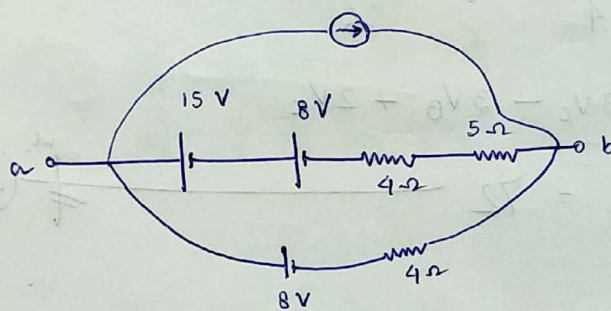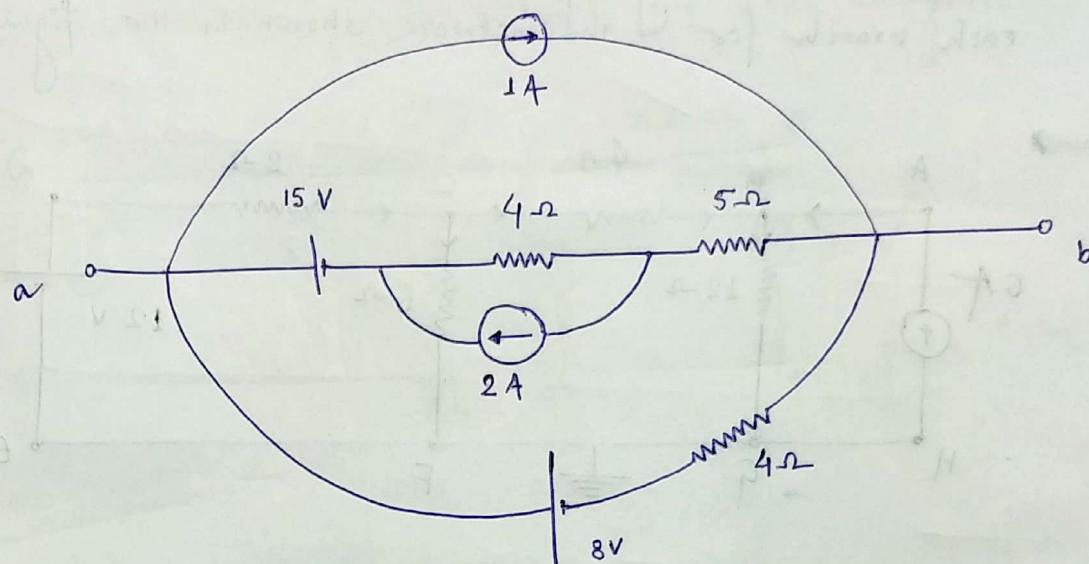Q7. Find the Thevenin's equivalent circuit for the circuit:—



$$R = \frac{9 \times 4}{9 + 4} = \frac{36}{13} \Omega$$


$$R = 2.77 \Omega$$

$$V_{Th} = 3.55 \times 2.77 \text{ V}$$

$$V_{Th} = 9.8335 \text{ V}$$

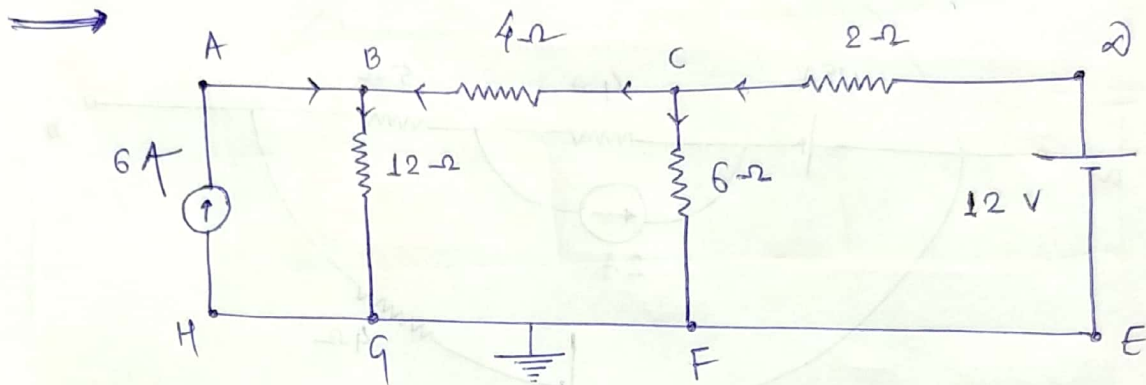Q.9.

Write the node voltage equations and determine the currents in each branch for the network shown in the figure.



At C

$$\frac{12 - V_C}{2} = \frac{V_C - V_B}{4} = \frac{V_C - 0}{6}$$

$$\Rightarrow 72 - 6V_C = 3V_C - 3V_B + 2V_C$$

$$\Rightarrow 11V_C - 3V_B = 72 \quad \text{eqn. (1)}$$

At B

$$6 + \frac{V_C - V_B}{4} = \frac{V_B - 0}{12}$$

$$\Rightarrow 72 + 3V_C - 3V_B = V_B$$

$$\Rightarrow 4V_B - 3V_C = 72 \quad \text{eqn. (2)}$$

Solving eqn. (1) and (2), we get,


$$\boxed{\begin{aligned} V_B &= 28.8 \text{ V} \\ V_C &= 14.4 \text{ V} \end{aligned}}$$

$$i_{12\Omega} = \frac{V_B - 0}{12} = \frac{28.8}{12} = 2.4 \text{ A}$$

$$i_{4\Omega} = 3.6 \text{ A}$$

$$i_{6\Omega} = 2.4 \text{ A} \quad \text{and} \quad i_{2\Omega} = 1.2 \text{ A}$$

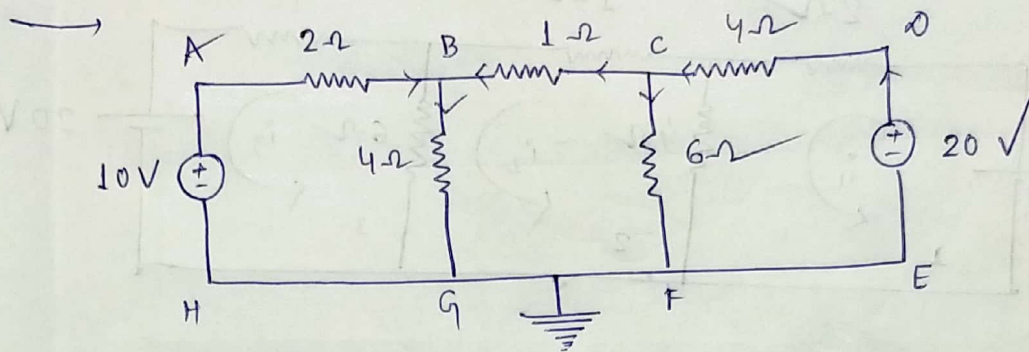Q.10. Verify the Kirchhoff's Law both (KCL and KVL) for the circuit shown in figure by mesh and nodal analysis.



Nodal analysis :-

At B :

$$\frac{10 - V_B}{2} + \frac{V_C - V_B}{1} = \frac{V_B - 0}{4}$$

$$\Rightarrow 20 - 2V_B + 4V_C - 4V_B = V_B$$

$$\Rightarrow 7V_B - 4V_C = 20 \quad \text{--- eqn (1)}$$

At C :-

$$\frac{20 - V_C}{4} = \frac{V_C - V_B}{1} + \frac{V_C - 0}{6}$$

$$\Rightarrow 60 - 3V_C = 12V_C - 12V_B + 2V_C$$

$$\Rightarrow -12V_B + 17V_C = 60 \quad \text{--- eqn (2)}$$

Solving eqⁿs (1) & (2),


$$\boxed{\begin{matrix} V_B = 8.17 \text{ V} \\ V_C = 9.29 \text{ V} \end{matrix}}$$

$$i_{2\Omega} = 0.91 \text{ A}$$

$$i_{1\Omega} = 1.12 \text{ A}$$

$$i_{4\Omega} = 2.67 \text{ A}$$

Similarly, by mesh analysis :-

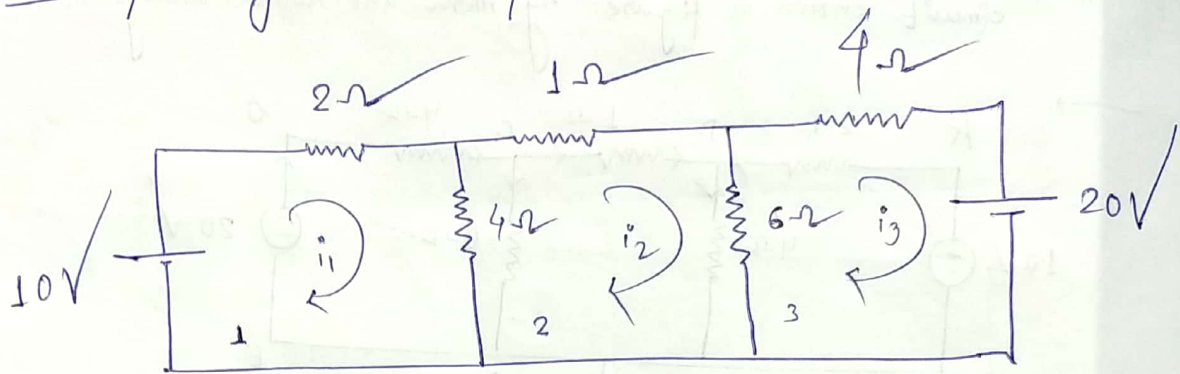

Loop-1 :

$$10 - 2i_1 - (i_1 - i_2) \cdot 4 = 0$$

$$\Rightarrow 10 - 6i_1 + 4i_2 = 0$$

$$\Rightarrow 3i_1 - 2i_2 = 5 \quad \text{--- eqn (1)}$$

Loop-2 :

$$-4(i_2 - i_1) - i_2 - (i_2 - i_3) \cdot 6 = 0$$

$$\Rightarrow 4i_1 - 11i_2 + 6i_3 = 0 \quad \text{--- eqn (2)}$$

Loop-3 :

$$-(i_3 - i_2) \cdot 6 - 4i_3 - 20 = 0$$

$$\Rightarrow 6i_2 - 10i_3 = 20 \quad \text{--- eqn (3)}$$

Solving eq^{ns} (1), (2), (3), we get :-

$$\begin{cases} i_1 = 0.91 \text{ A} \\ i_2 = -1.12 \text{ A} \\ i_3 = -2.67 \text{ A} \end{cases}$$

Comparing the values of current in 2 processes :-

$$i_{2\Omega} = i_1 = 0.91 \text{ A}$$

$$i_{4\Omega} = i_3 = 2.67 \text{ A}$$

$$i_{1\Omega} = i_2 = 1.12 \text{ A}$$

∴ We can compare more, but from these 3 values, we can say that KCL & KVL are verified by the nodal and mesh-analysis methods.

Q. 11. A series RLC circuit consists of $R = 1000 \Omega$,
 $L = 100 \text{ mH}$ and $C = 10 \text{ pico farads}$. The applied voltage
 across the circuit is 100 V .

$$R = 1000 \Omega; \quad L = 100 \times 10^{-3} \text{ H}; \quad C = 10 \times 10^{-12} \text{ F}; \quad V = 100 \text{ V}$$

(i) Condition for resonance, $X_L = X_C$

$$X_L = L\omega$$

$$= 10^{-1} \times 10^6$$

$$\therefore X_L = 10^5$$

$$\therefore L\omega = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$\Rightarrow \omega = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{10^{-1} \times 10^{-11}}} = \frac{1}{10^{-6}}$$

$$\therefore \boxed{\omega = 10^6 \text{ rad s}^{-1}}$$

$$(ii) \text{ Quality factor} = \frac{\text{Power stored}}{\text{power dissipated}} = \frac{\frac{1}{2} I^2 X_L}{\frac{1}{2} I^2 R} = \frac{\frac{1}{2} I^2 X_C}{\frac{1}{2} I^2 R} \left[\because X_L = X_C \right]$$

$$= \frac{X_L}{R} = \frac{X_C}{R} = \frac{10^5}{10^3} \text{ Hz}$$

$$\therefore Q. \text{ factor} = 100 \text{ Hz}$$

(iii) Angular frequency at half power points:

• lower cut-off frequency:-

$$\omega_L = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= -\frac{10^3}{2 \times 10^{-1}} + \sqrt{\left(\frac{10^3}{2 \times 10^{-1}}\right)^2 + \frac{1}{10^{-12}}}$$

$$\therefore \omega_L = -\frac{10^4}{2} + 10^4 \sqrt{\frac{1}{4} + 10^4}$$

• Higher cut-off frequency:-

$$\omega_C = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\therefore \omega_C = \frac{10^4}{2} + 10^4 \sqrt{\frac{1}{4} + 10^4}$$

$$(iv) \text{ Bandwidth } = \frac{f_r}{Q}$$

$$= \frac{\omega}{2\pi Q} = \frac{10^6}{2\pi \times 10^2}$$

$$= \frac{10^4}{2\pi}$$

Q. 12. A voltage, $V = 100 \sin 314t$ is applied to a circuit consisting of a $25\text{-}\Omega$ resistor and an 80 microfarad capacitor in series. Determine the following :-

$$V = 100 \sin(314t)$$

$$R = 25\text{-}\Omega; \quad C = 80 \times 10^{-6} \text{ F}$$

$$Z = \sqrt{625 + 6400 \times 10^{-12}} \Omega$$

$$\approx \sqrt{625} \Omega$$

$$\approx 25 \Omega$$

$$\text{Also, } i_m = \frac{V_m}{Z}$$

$$= \frac{100}{25} \text{ A}$$

$$i_m = 4 \text{ A}$$

$$i = 4 \sin(314t + 57.8^\circ)$$

$$\text{Also, } \tan \phi = \frac{X_C}{R} = \frac{1}{\omega RC}$$

$$= \frac{1}{314 \times 80 \times 10^{-6} \times 25}$$

$$= 1.592$$

$$\phi = \tan^{-1}(1.592)$$

$$\phi = 57.8^\circ$$

∴ Reqd. expression : —

$$i = 4 \sin(314t + 57.8^\circ) \quad \text{ans.}$$

(ii) Power consumed = $\frac{V_i}{2} \cos \phi$

$$= \frac{100 \times 4^2}{2} \cos(57.8^\circ) \text{ W}$$

$$= 200 \times (0.532) \text{ W}$$

$$= 106.4 \text{ W} \quad \text{ans.}$$

(iii) $V = i \cdot X_C$ $i = \frac{i_m}{2} = 2 \text{ A}$

$$= 2 \times \frac{1}{\omega C}$$

$$= 2 \times \frac{1}{314 \times \frac{80}{40} \times 10^{-6}} \text{ V}$$

$$= 79.6 \text{ V} \quad \text{ans.}$$

End