

Ex. No.:3

Date: 10/10/19

## Response of RLC Series Circuit


Aim: To determine and verify the resonant current & resonant frequency for the given RLC circuit by theoretical and simulation values.

Apparatus/Tool required:


ORCAD / Capture CIS --> Analog Library - R, L & C  
Source Library - Vac  
Ground (GND) - 0 (zero)

Simulation Settings: Analysis Type - Transient (Time Domain)  
Run to time: 20ms



Circuit Diagram:

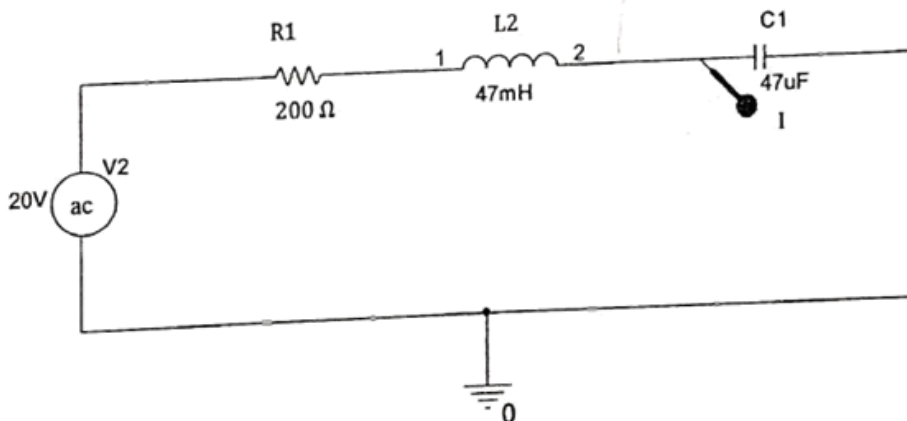


Theory:

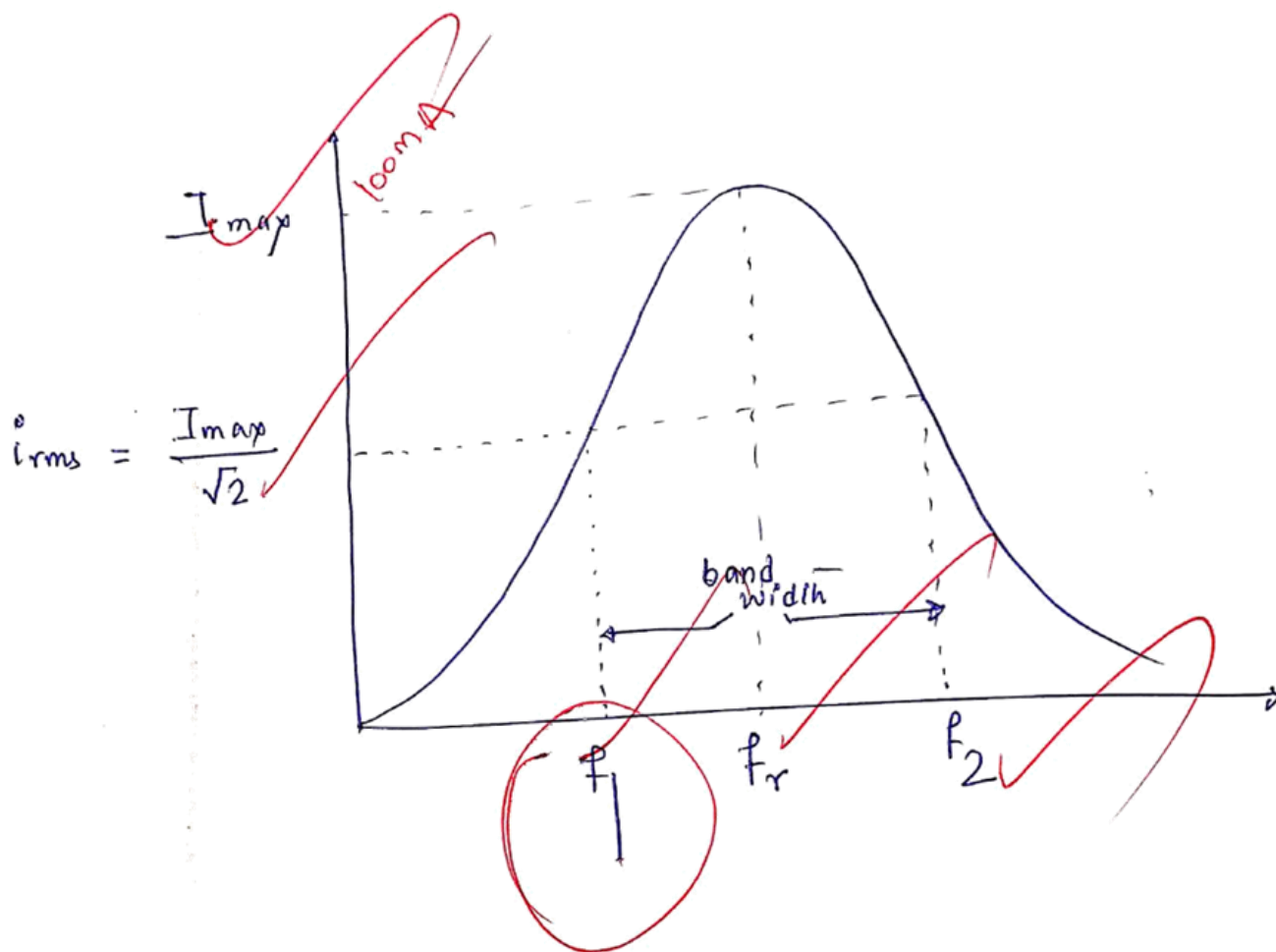


## Circuit Diagram & Graph:

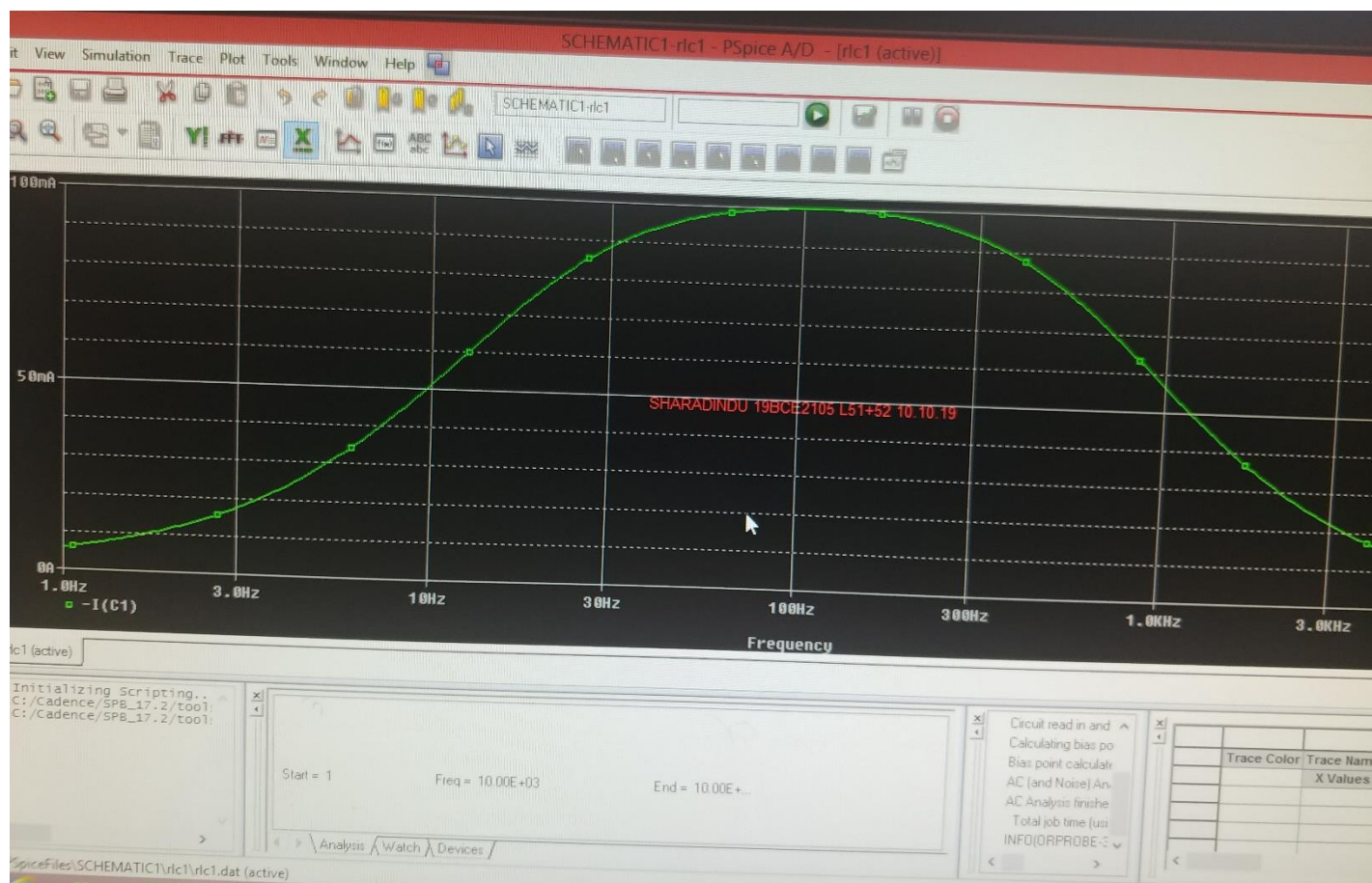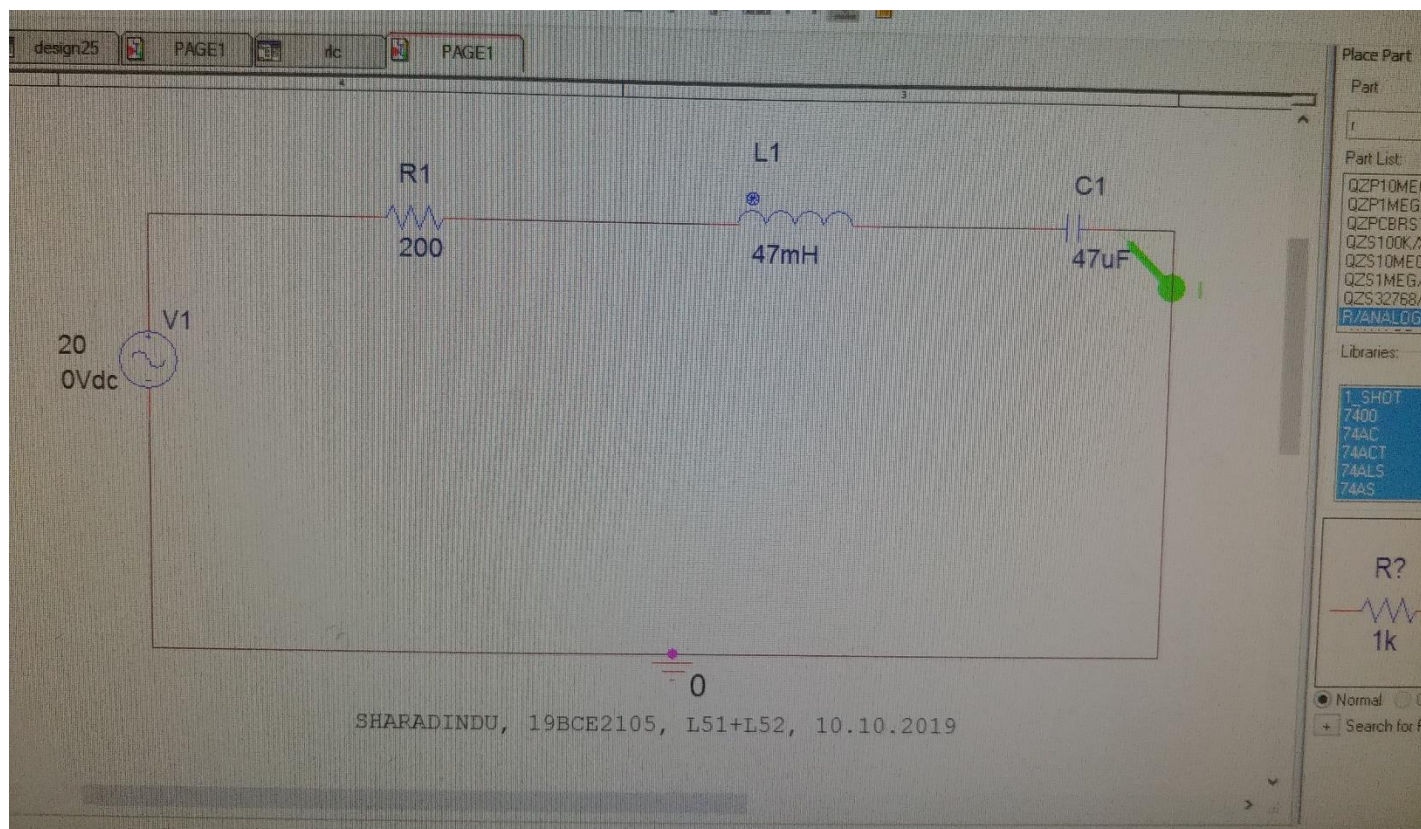

## Circuit Diagram & Graph (..contd.):

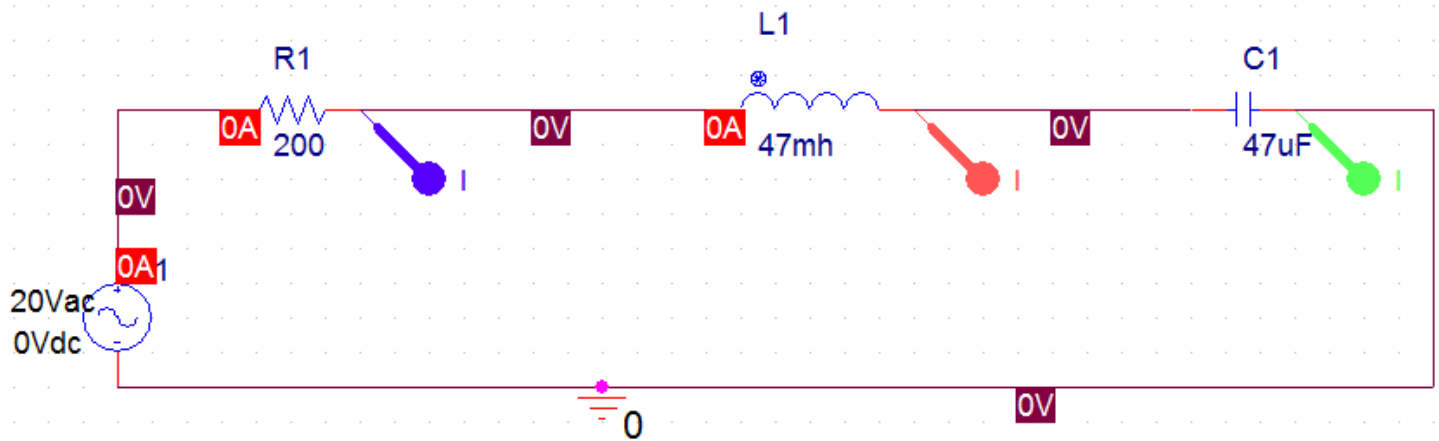

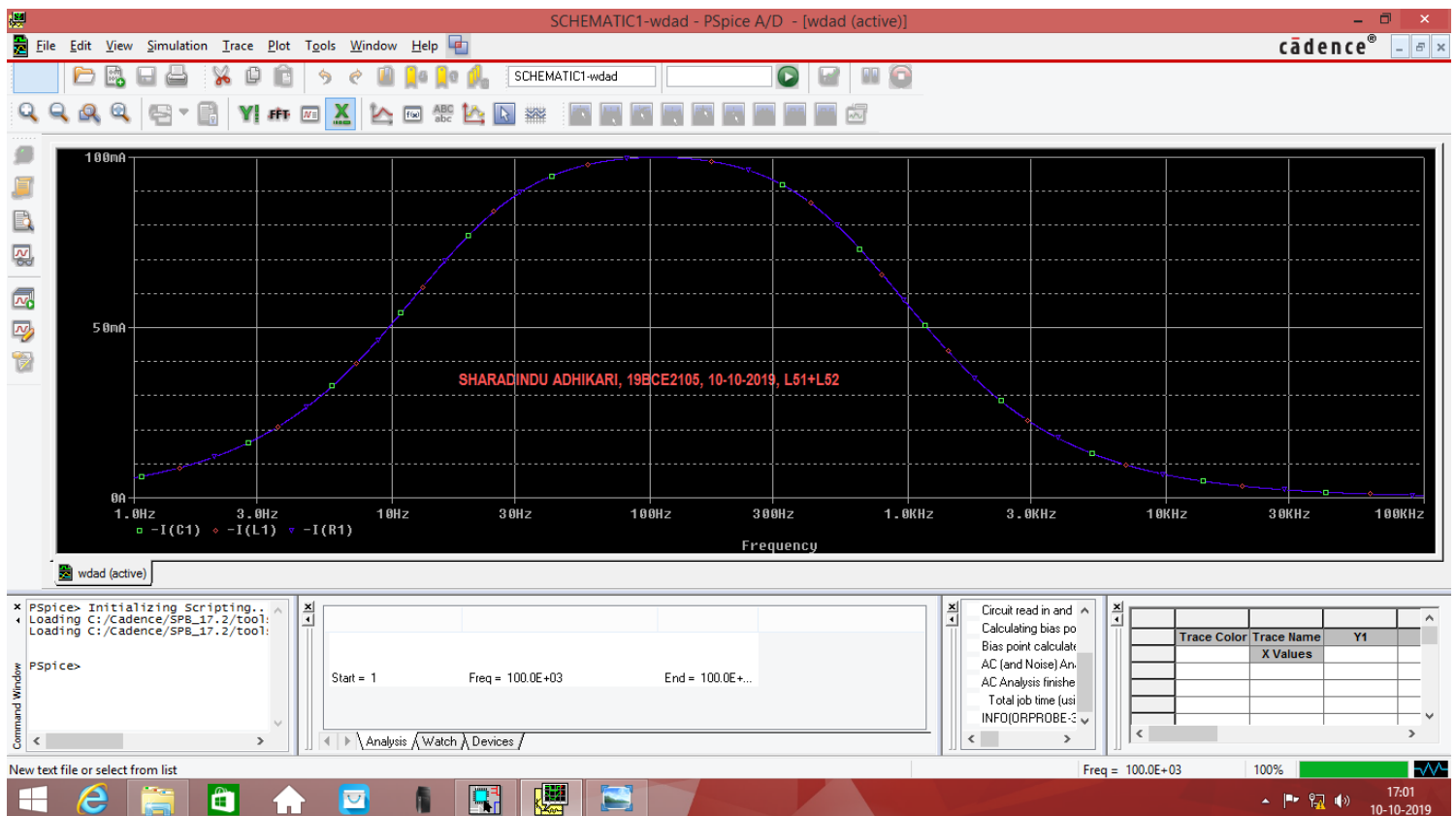SHARADINDU ADHIKARI, 19BCE2105, 10-10-2019, L51+L52





Formulae :

$$i = \frac{V}{Z} = \frac{V}{R (= Z_r)}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$i = \frac{V}{Z}$$

$$X_L = X_C$$

$$Z_r = R$$

Calculation:

$$X_{Lr} = X_{Cr}$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$4\pi^2 f_r^2 LC = 1$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$f_r = \frac{\sqrt{1}}{\sqrt{4\pi^2 LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{47 \times 10^{-3} \times 47 \times 10^{-6}}}$$

$$f_r = 107.1 \text{ Hz}$$

$$\therefore Q\text{-factor} > 200$$

$$i_r = \frac{V}{Z} = \frac{V}{Z_r (= R)}$$


$$i_r = \frac{20}{200} \text{ Amp}$$

$$i_r = 0.1 \text{ Amps}$$


$$[i_r = 100 \text{ mAmps}]$$

$$\therefore Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Model Graph:

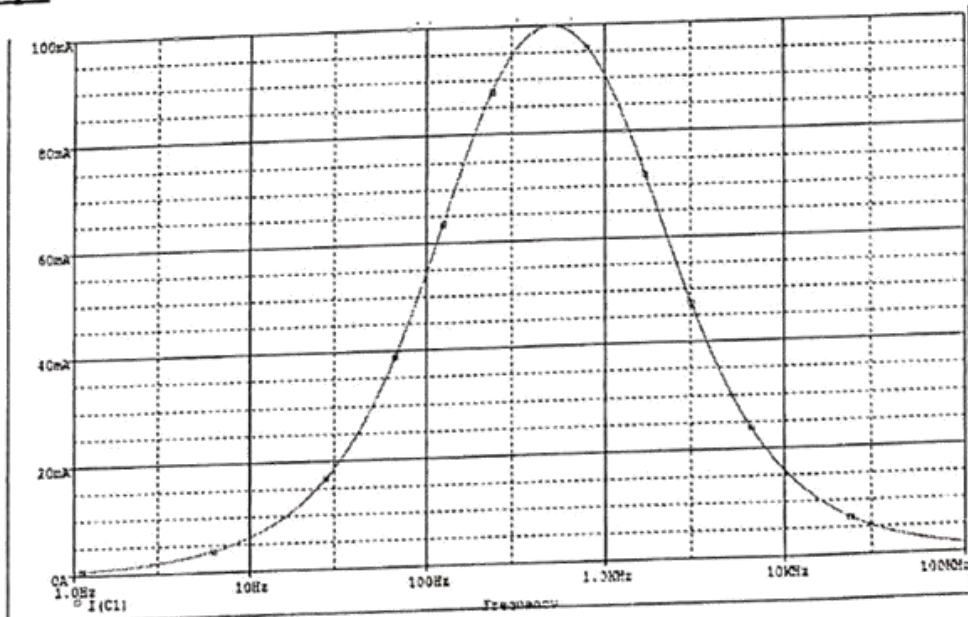
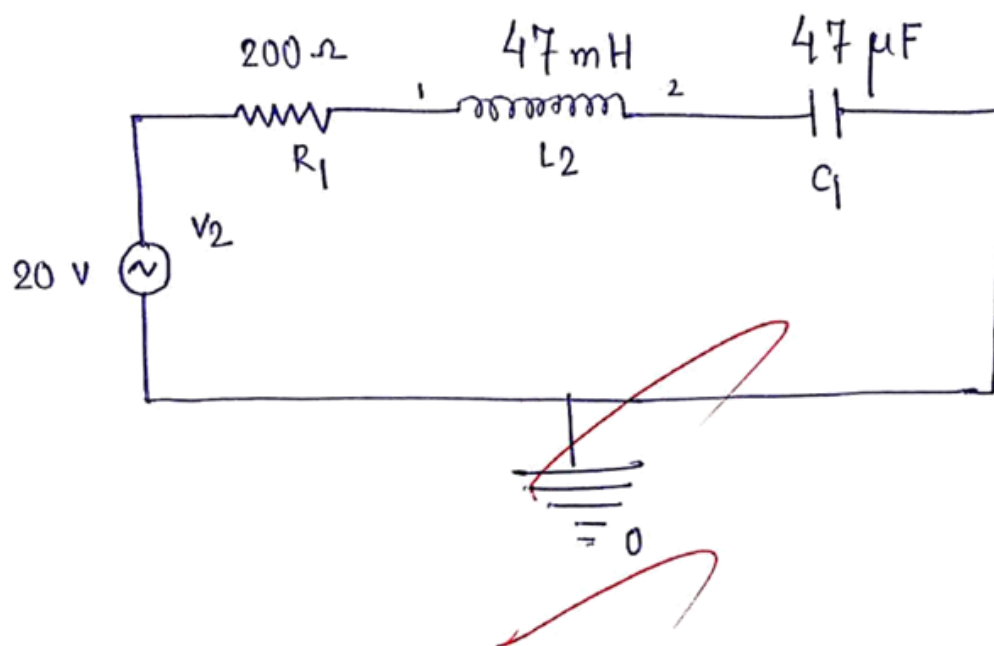
### Simulation Circuit Diagram and Output:



$$i_r = 100 \text{ mA}$$

$$f_r = 107.1 \text{ Hz}$$

Procedure:-

~~10/10/19~~  
~~Sharadindu~~

Result:- The series resonance RLC circuit have been performed in CIS capture as simulation and the following theoretical and simulation values are tabulated:-

parameter	Theoretical values	Simulation values
$i_r$	100 mA	100 mA
$f_r$	107.1 Hz	107.1 Hz

Reg. No: 19 BCE2105 Name: SHARADINDU A. Date: 10/10/2019