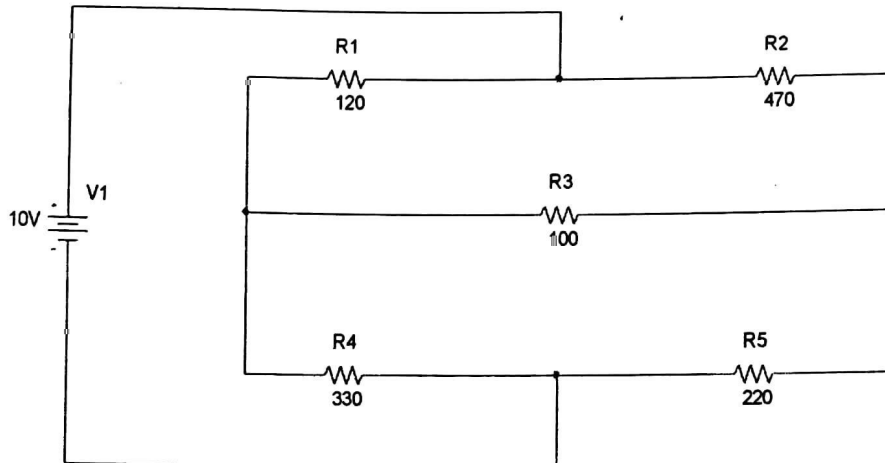


Verification of Thevenin's Theorem

Aim: To verify the Thevenin's Theorem of a given network by theoretical and experimental values.

Circuit Diagram



Apparatus/Tool required:

Sl. No.	Components Name	Range	Quantity
1	Resister	120Ω, 330Ω, 470Ω, 220Ω, 100Ω	Each 1 No.
2	Ammeter	0-50mA (DC)	1 No.
3	Voltmeter	0-10V (DC)	1 No.
4	RPS	0-32 V (DC)	1 No.
5	Connecting Wires	-	Few
6	Bread Board	-	1 No.


Theory

Statement: Thevenin's Theorem

~~The~~ linear bilateral network with output terminals A and B can be replaced by a single voltage source in series with equivalent resistance.

Hardware Circuit:


To Find V_{TH} :

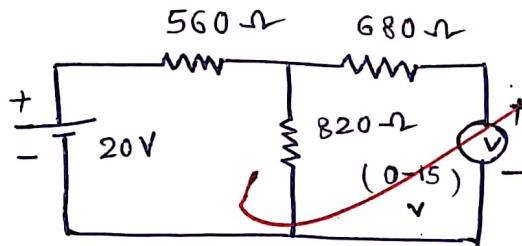

Reading:

Applied Voltage (Volts)	V_{TH} (Volts)
10 V	5.25 V

To Find R_{TH} :

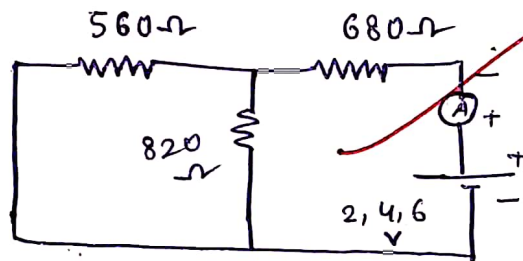


Reading:

Applied Voltage	Voltmeter Reading	Ammeter Reading	$R_{TH} = V/I$ ohms
2 V		1.9 mA	1.05 K Ω
4 V		3.8 mA	1.05 K Ω
6 V		5.6 mA	1.07 K Ω

Average of $R_{TH} = 1.05 K \Omega$.

To Find I_L :

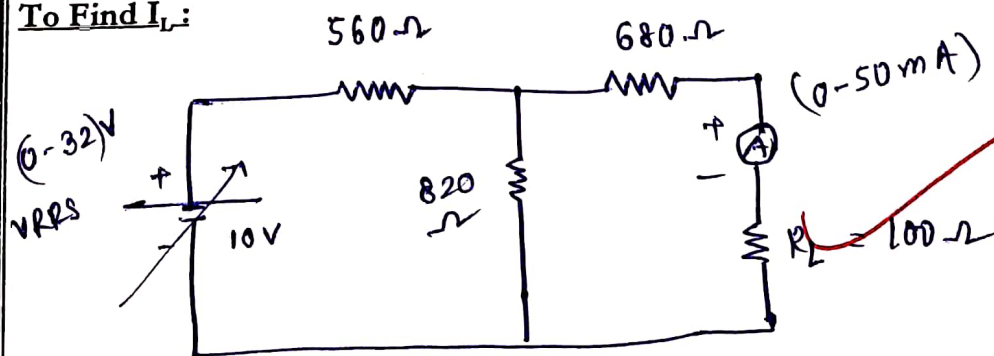


Reading:

Applied Voltage (Volts)	Ammeter Reading (Amps)
10 V	5.25 mA

Manual Calculations:

To Find V_{TH} :

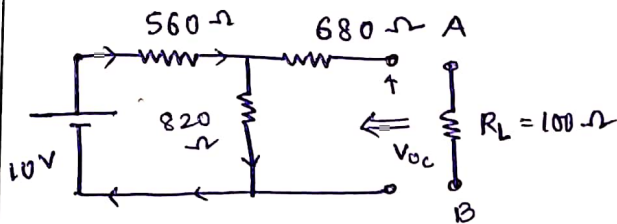

$$V_{OC} = V_{TH} = V_{AB}$$

$$i = \frac{V}{R_T} = \frac{10}{560 + 820}$$

$$= 7.2 \text{ mA}$$


$$i = 7.2 \times 10^{-3} \text{ A}$$

$$V_{TH} = V_{OC} = V_{AB} = i_{820\Omega} \times R_L$$

$$= 7.2 \times 10^{-3} \text{ V} \times 820$$

$$V_{TH} = 5.9 \text{ V}$$

To Find R_{TH} :

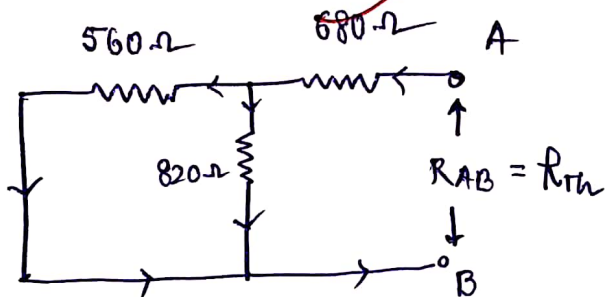


$$R_{TH} = R_{AB} = (560 \parallel 820) + 680 \Omega$$

$$= \frac{560 \times 820}{560 + 820} + 680 \Omega$$

$$R_{TH} = 1012.75 \Omega$$

To Find I_L :

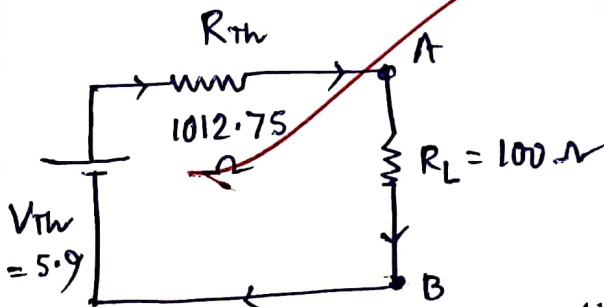

$$i_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{5.9}{1012.75 + 100} \text{ mA}$$

$$i_L = 5.3 \text{ mA}$$

Procedure:

Results : The Thevenin's Theorem has been verified for the given network both by theoretically & experimentally & the following results are tabulated as under:—

Result: ~~Thevenin~~

Thevenin's Theorem

parameters

V_{Th}

R_{Th}

i_L

Manual Calculations

[Theoretical values]

5.9 V

1012.75 Ω

5.3 mA

Practical Output

[Experimental values]

5.25 V

1050 Ω

5.25 mA

Inference:

Verified

Reg. No: 19 BCE 2105

Name: SHARADINDU
ADHIKARI

Date: 8/8/2019